



**Future Technology Devices International Ltd.**

## **Application Note**

**AN\_143**

# **Auto Sensing And Isolation Design For RS232/RS422/RS485 Interfaces**

**Document Reference No.: FT\_000270**

**Version 1.0**

**Issue Date: 2010-05-26**

This application note explains how to design auto mode sensing for RS232, RS485 and RS422 interfaces. It also describes how to implement isolation of these interfaces. The examples of auto mode sensing require two different connectors, one for RS232 and another for RS422/485.

Only one protocol interface can operate at any one time.

**Future Technology Devices International Limited (FTDI)**

Unit 1,2 Seaward Place, Glasgow G41 1HH, United Kingdom

Tel.: +44 (0) 141 429 2777 Fax: + 44 (0) 141 429 2758

E-Mail (Support): [support1@ftdichip.com](mailto:support1@ftdichip.com) Web: <http://www.ftdichip.com>

Copyright © 2009 Future Technology Devices International Limited

## Table of Contents

<b>1</b>	<b>Introduction .....</b>	<b>2</b>
<b>2</b>	<b>Implementing RS232/RS422/RS485 Auto-Sensing .....</b>	<b>3</b>
2.1	RS232/RS422/RS485 Auto-Sensing reference design .....	3
2.2	RS422/RS485 Auto-Sensing reference design .....	7
2.3	Termination Resistors .....	10
<b>3</b>	<b>Implementing RS232/RS422/RS485 Isolation .....</b>	<b>11</b>
3.1	Isolated RS232 System .....	11
3.2	Isolated RS422 System .....	13
3.3	Isolated RS485 System .....	15
<b>4</b>	<b>Contact Information .....</b>	<b>18</b>
	<b>Appendix A – List of Figures and Tables .....</b>	<b>20</b>
	<b>Appendix B – Revision History .....</b>	<b>21</b>

## **1 Introduction**

This application note explains how to combine RS232, RS485 and RS422 functions into one product and how to auto sense which interface is being used. Any application should have two different connectors, only one of which can be used at any one time: one for RS232 and one for RS422/485. It also explains how to implement isolated RS232/422/485 interfaces in system.

The example schematics are given are for illustration purposes only.


## **2 Implementing RS232/RS422/RS485 Auto-Sensing**

The following example illustrates one possible solution to auto-sense the RS232/422/485 interface. Any application requires two different connectors: one for RS232 and another for RS422/485. Only one connector can be in use at any one time.

### **2.1 RS232/RS422/RS485 Auto-Sensing reference design**

When designing the RS232, RS485 and RS422 interfaces in one circuit, care must be taken with the receiver source since it can be from any one of the three interface converter's output pins. These cannot be simply shorted together.

In this case, it is necessary that these three interface outputs are maintained at a high state when they are idle, and use an AND gate to sense the interface sources. This is illustrated in the following diagram.

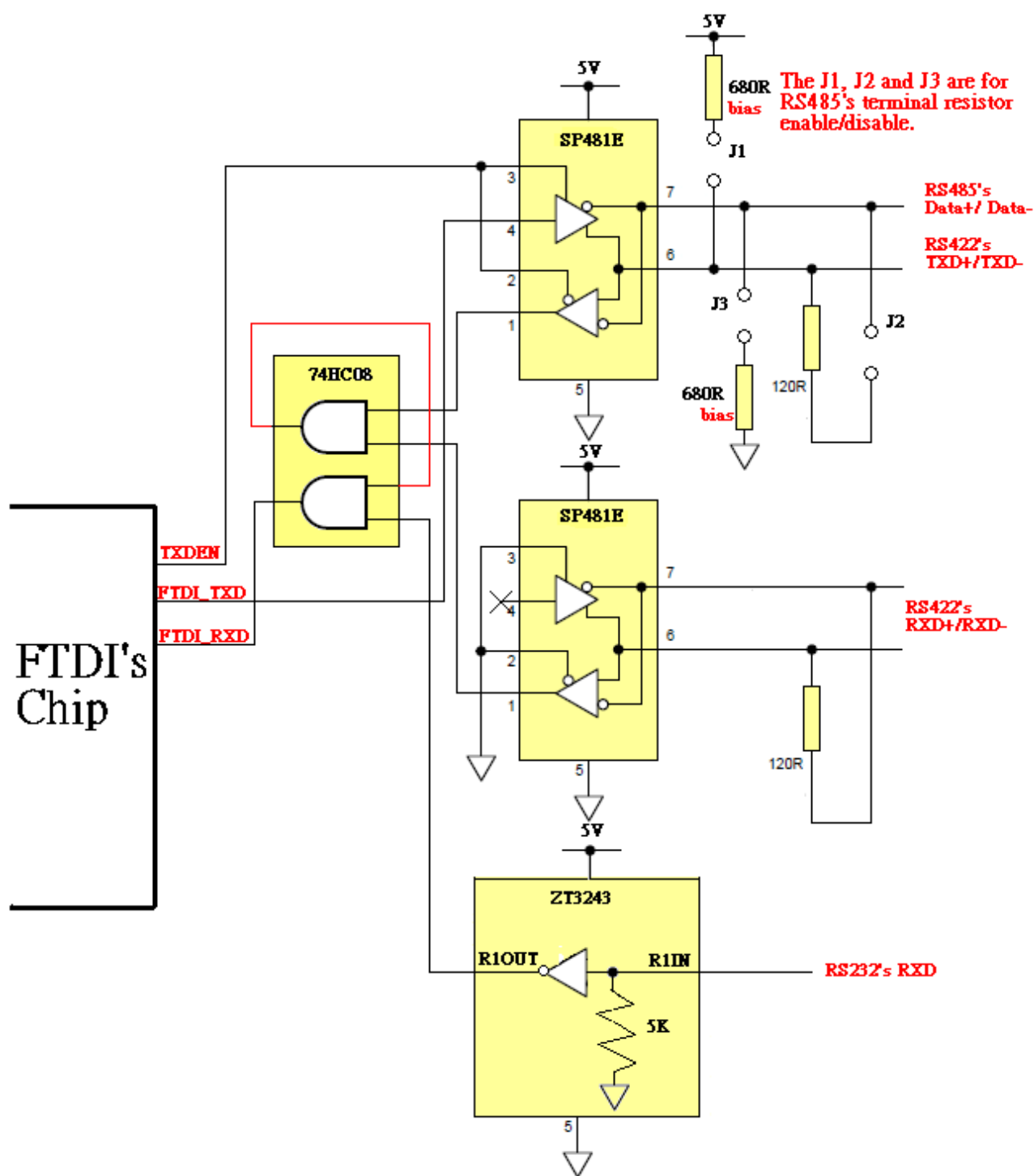

**Figure 2-1 RS232/RS422/RS485 Auto Sensing Block Diagram**

As shown, it is necessary to add some bias resistors to guarantee that the RS422/485 interfaces output a high state when the interfaces are idle. The ZT3243, the converter for RS232 interface, has an internal 5K $\Omega$  pull-down resistor, which forces the R1OUT output to a high state when the RS232 bus is idle. The AND gate is used to link the three received sources into FTDI RXD pin. The result is that the correct data

is received no matter which interfaces is being used. The limitation is that only one interface can be used at any one time.

The same method is suitable for the CTS received signal.

**Notes.**

1. When using FT232R and FT4232H in RS485 mode, it is necessary to program the EEPROM to enable the TXDEN function.
2. In the reference design, RS485 cannot support echo function since it will cause data overlap when in the RS422 mode.
3. The jumpers (J1, J2 and J3) are reserved to enable terminal and bias resistors. Mounting the jumpers (J1, J2 and J3) will enable the 120 Ohm termination and 680 Ohm bias resistors. The below section (CH2.3) shows the details with termination resistor. The terminator function has to be enabled when the device is connected at the end of a cable in RS485 mode.

A completed reference design example is given in Figure 2-2


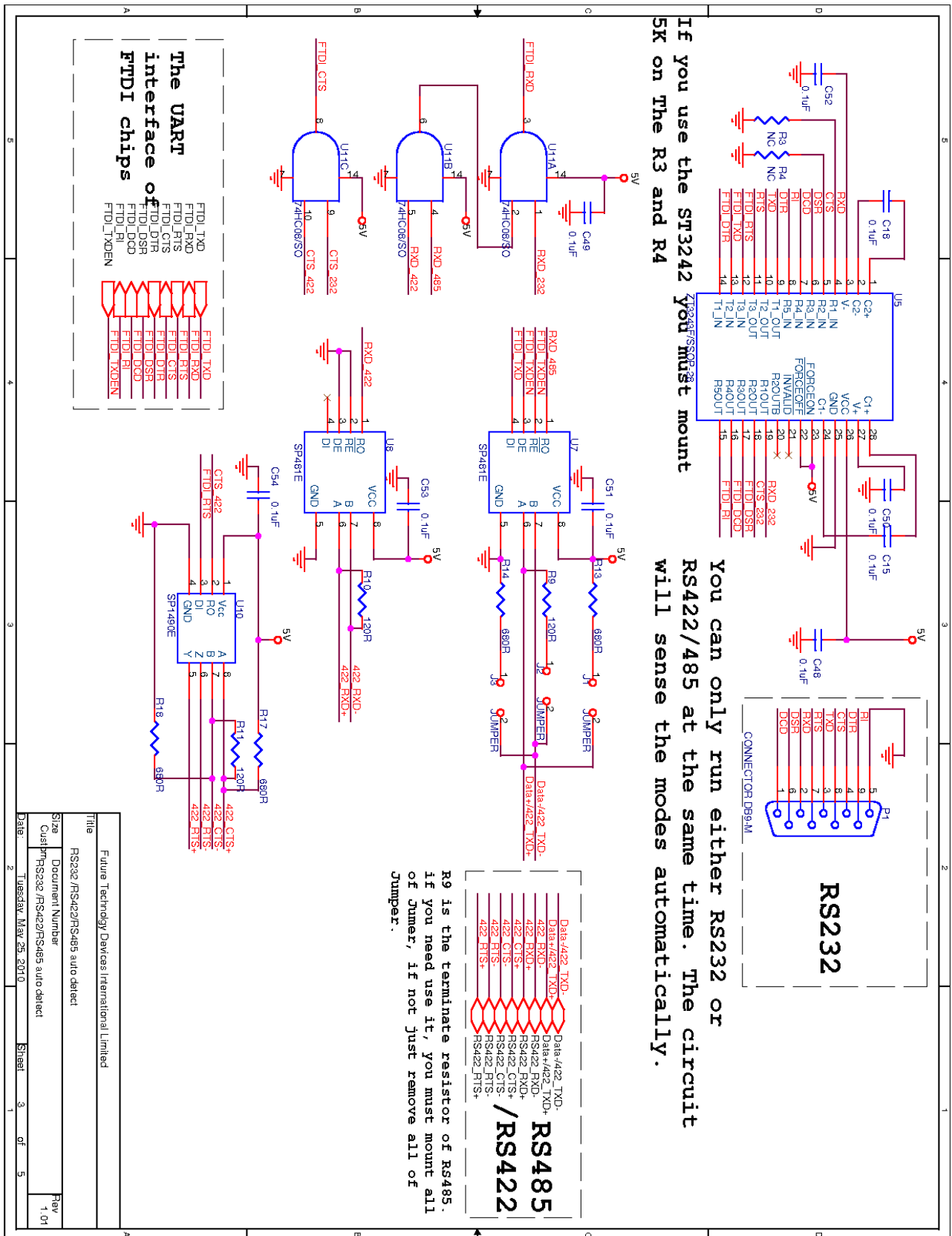


Figure 2-2 Reference Design 1 – RS232/RS422/RS485 Auto-sensing

## 2.2 RS422/RS485 Auto-Sensing reference design

If auto-sensing is only required between RS422 and RS485, then the example shown in Figure 2-3 can be used. This method is similar to the RS232/422/485 sensing method.

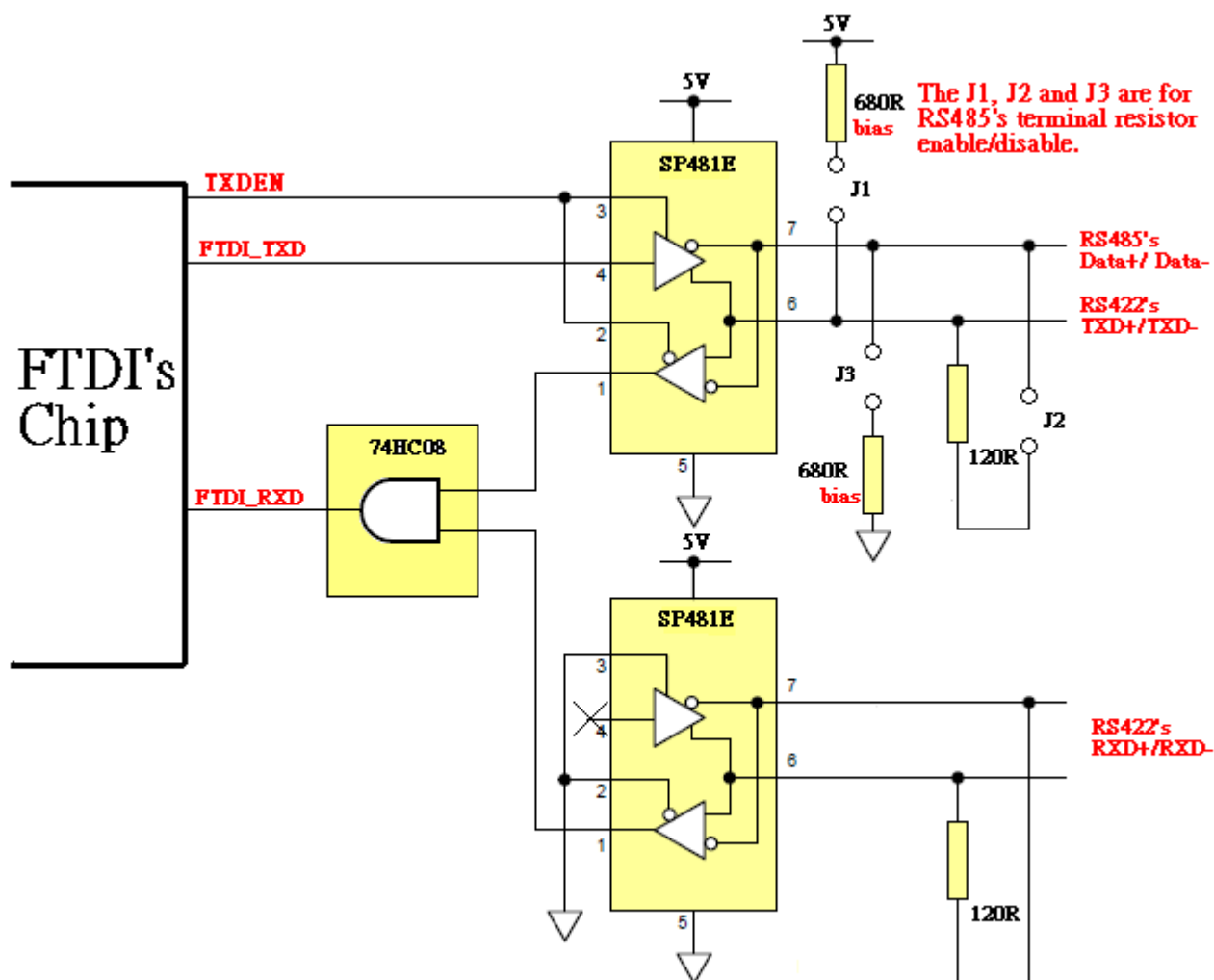

**Figure 2-3 RS485/RS422 Auto-Sensing Block Diagram**

Again, it is necessary to add some bias resistors to guarantee that the RS422/485 interfaces outputs are high when the interfaces are idle. The AND gate is used to link the two received sources into FTDI RXD pin. The result is that the correct data is received no matter which interfaces is being used. The limitation is that only one interface can be used at any one time.


### Notes.

1. When using FT232R and FT4232H in RS485 mode, it is necessary to program the EEPROM to enable the TXDEN function.



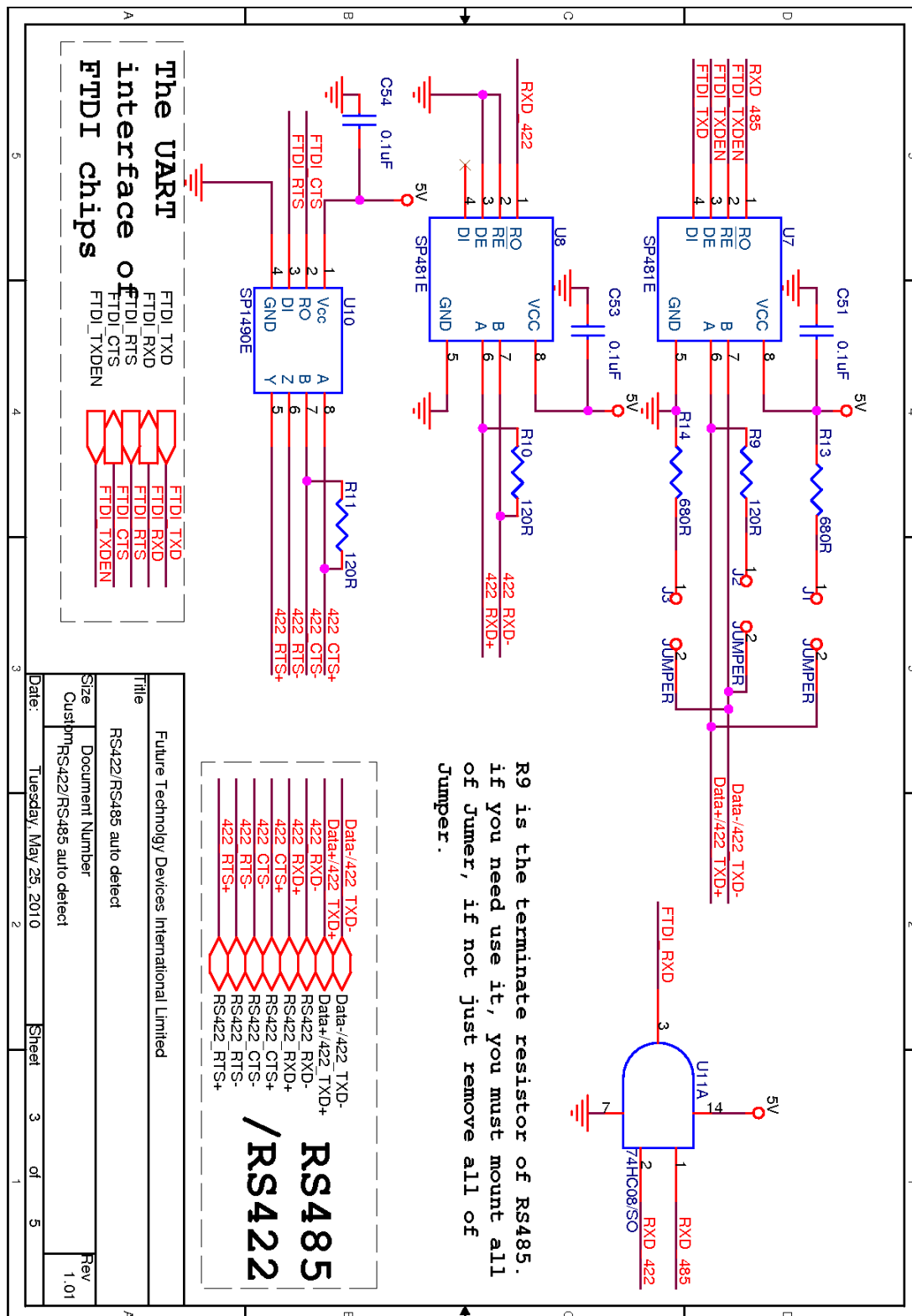2. In this design, RS485 cannot use echo mode since it will cause data overlap in the RS422 mode.
  
3. The jumpers (J1, J2 and J3) are reserved for terminal and bias resistors enabled. Mounting the jumpers (J1, J2 and J3) will enable the 120 Ohm termination and 680 Ohm bias resistors. The below section (CH2.3) shows the details with termination resistor. The terminator function has to be enabled when the device is connected at the end of cable in RS485 mode.

A completed reference design example is given in Figure 2-4.



### Figure 2-4 Reference Design 2 – RS422/RS485 Auto-sensing

## 2.3 Termination Resistors

The recommended arrangement of the wires is as a connected series of point-to-point (multi-dropped) nodes, a line or bus, not a star, ring, or multiply-connected network. Ideally, the two ends of the cable will have a termination resistor connected across the two wires. Without termination resistors, reflections of fast driver edges can cause multiple data edges that can cause data corruption. Termination resistors also reduce electrical noise sensitivity due to the lower impedance, and bias resistors are required. The value of each termination resistor should be equal to the cable impedance (typically, 120 Ohms for twisted pairs).

The reference circuit below illustrates a simple method to control the bias and terminal resistors without having to use jumpers. Normally, the terminator function has to be enabled when the device is connected at the end of cable in RS485 mode.

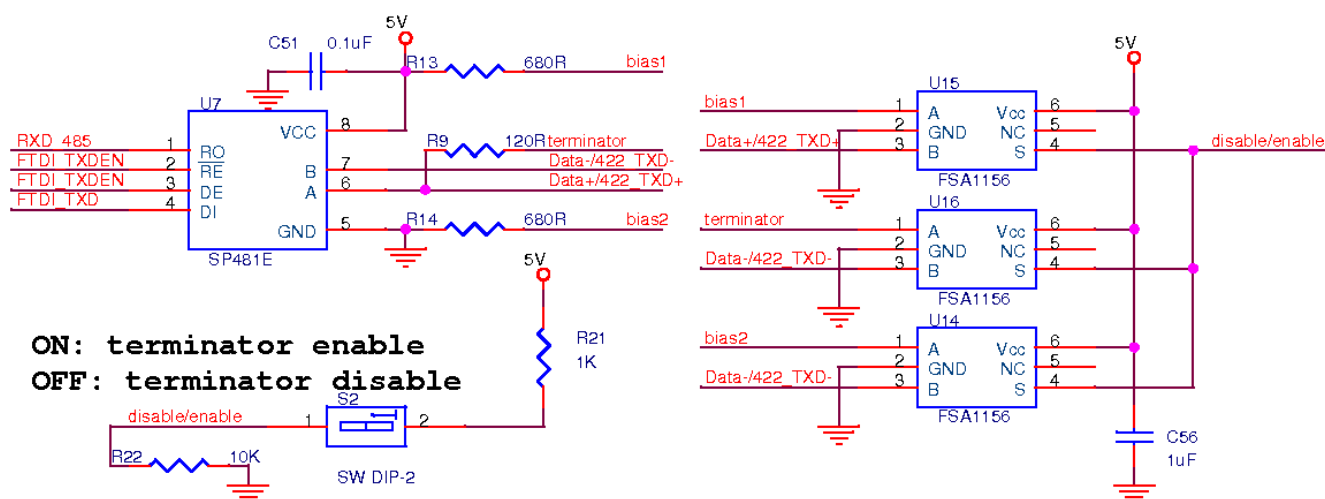


Figure 2-5 RS485's Termination Enable/Disable Control Circuit

### 3 Implementing RS232/RS422/RS485 Isolation

This chapter illustrates how to implement an isolated RS232/422/485 interface. It also shows how to implement the isolated power and ground. The independent power/ground/interface signals can help to avoid the abnormal coupling of noise back into the system.

#### 3.1 Isolated RS232 System

An example of how to isolate the RS232 interface is shown in Figure 3-1. The transformer is used to isolate the power source and the optical couplers are used to isolate the interface signals. Note that there are two independent grounds in the system.


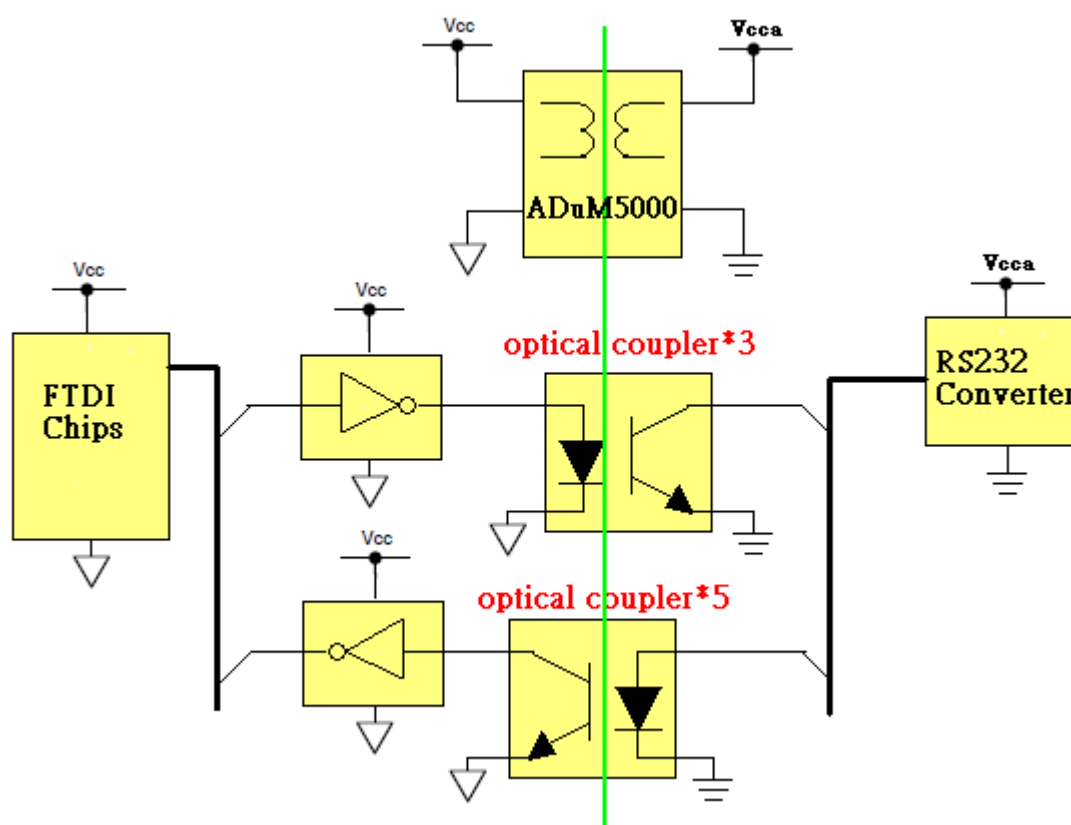


Figure 3-1 Block Diagram of RS232 Isolated

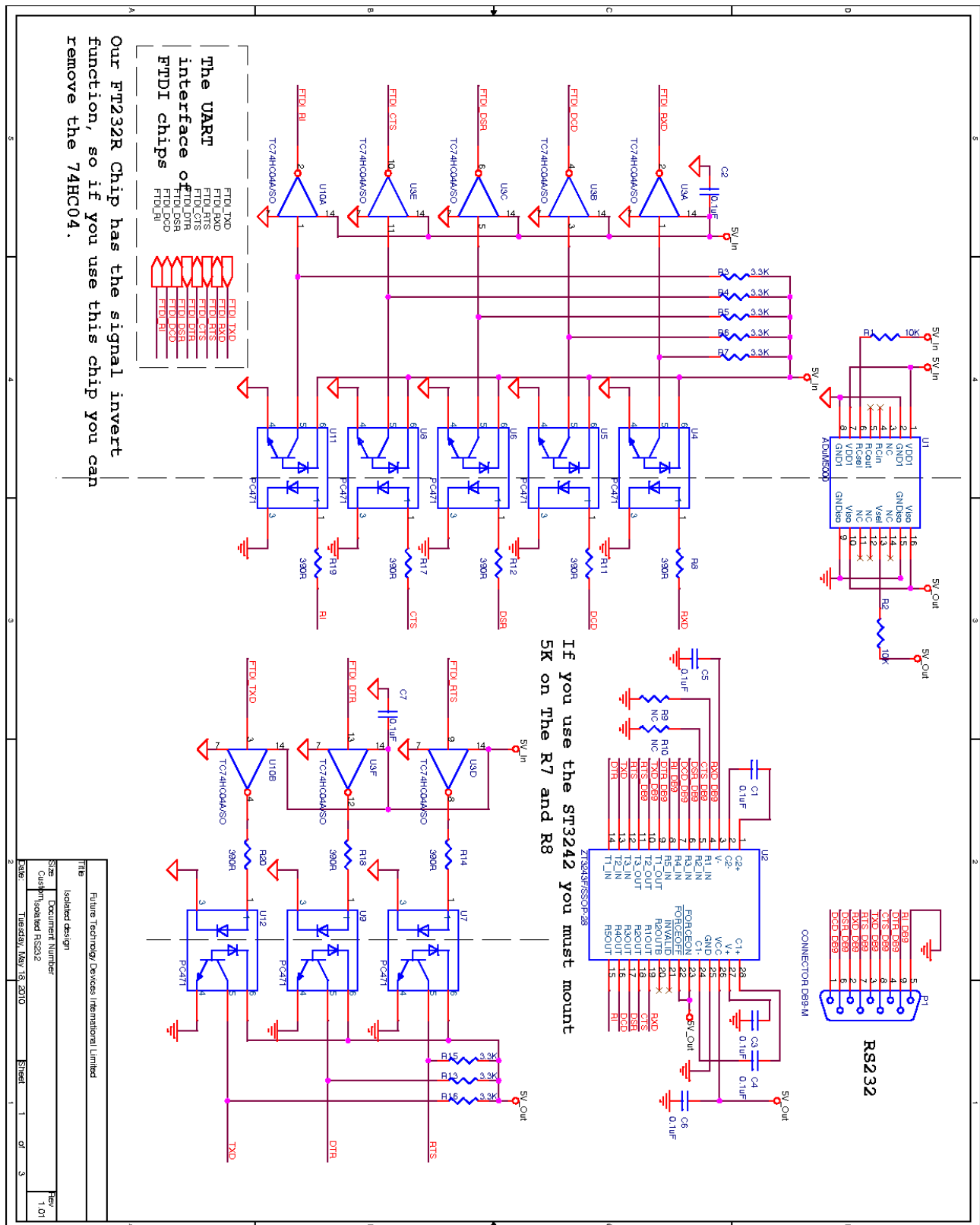A completed reference design example is given in Figure 3-2.



### Figure 3-2 Reference Design 3 – RS232 Isolation Implementation Example

### 3.2 Isolated RS422 System

An example of how to isolate an RS422 interface is shown in Figure 3-3. The transformer is used to isolate the power source and the optical couplers are used to isolate the interface signals. Note that there are two independent grounds in the system.

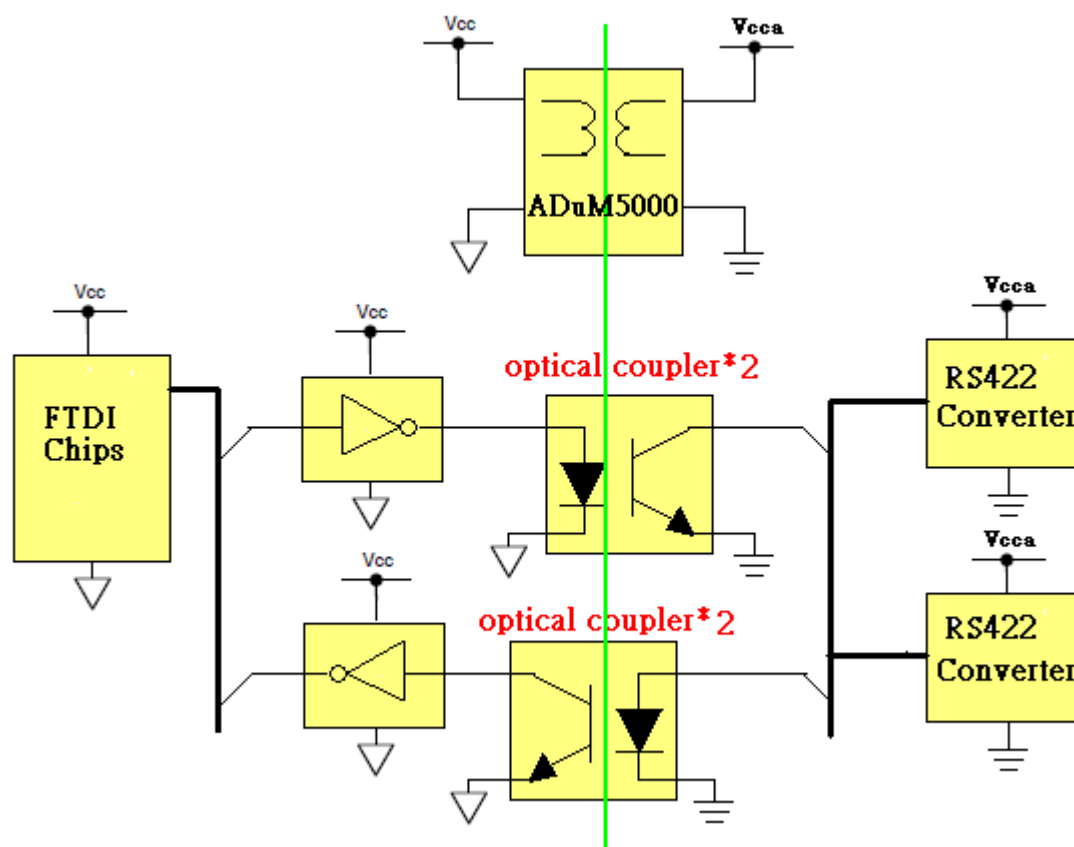


Figure 3-3 Block Diagram of RS422 Isolated

A completed reference design example is given in

Figure 3-4


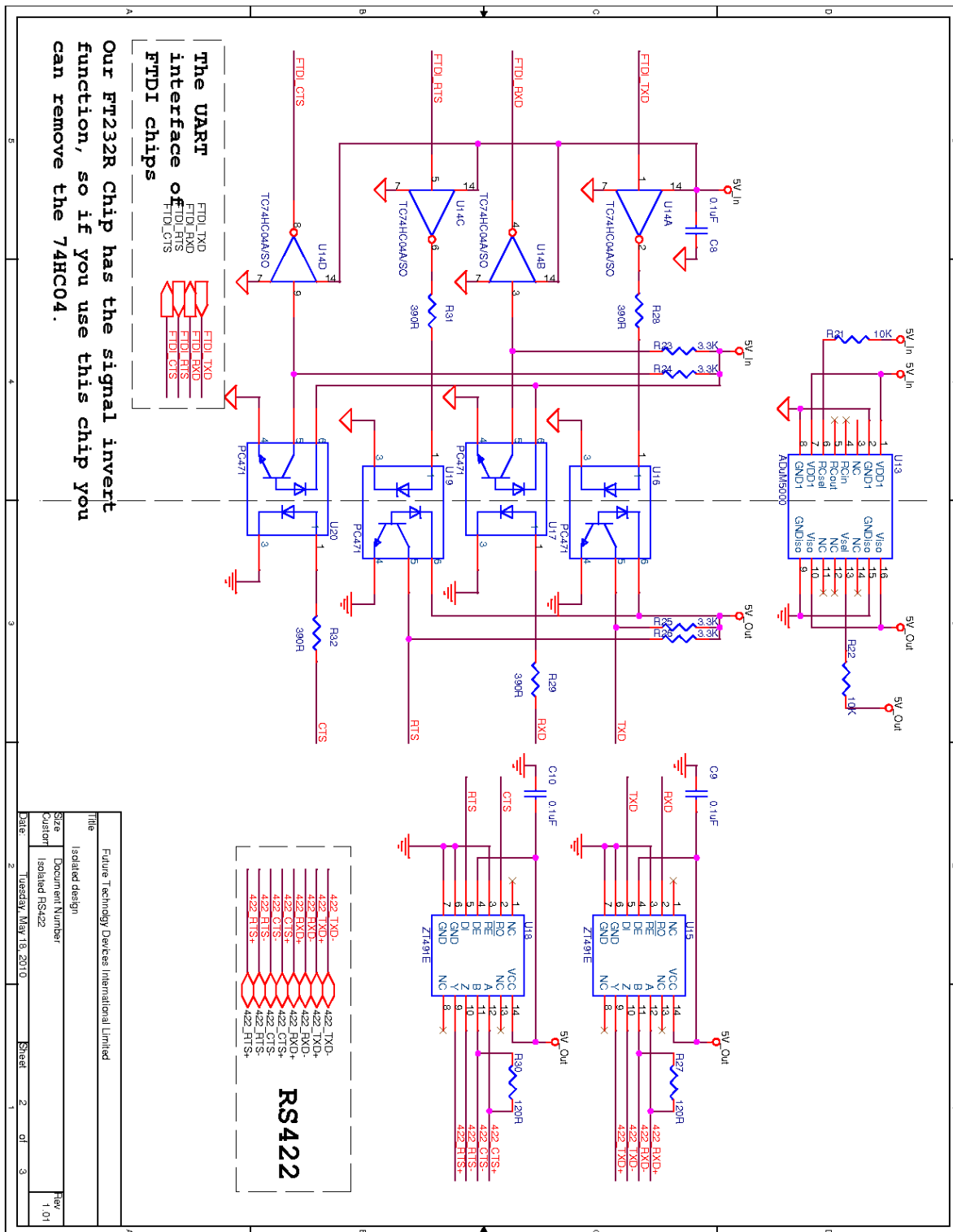


Figure 3-4 Reference Design 4 – RS422 Isolation Implementation Example

### 3.3 Isolated RS485 System

An example of how to isolate an RS485 interface is shown in Figure 3-5. The transformer is used to isolate the power source and the optical couplers are used to isolate the interface signals. Note that there are two independent grounds in the system.

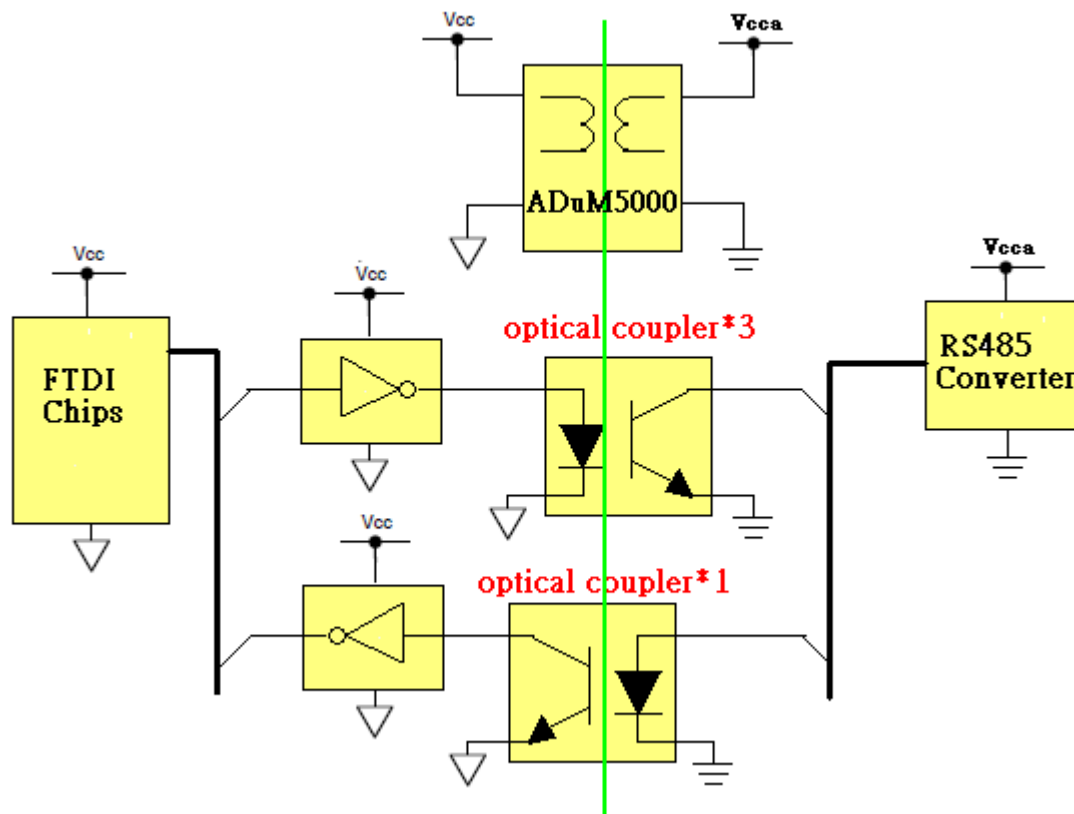


**Figure 3-5 Block Diagram of RS485 Isolated**

#### Notes.

1. When using FT232R and FT4232H in RS485 mode, it is necessary to program the EEPROM to enable the TXDEN function.
2. RS485 interface shown above has an echo function enabled. The jumper links shown in Figure3-6 can be used to enable or disable this function. If using an FT232R, it is possible to use one CBUS pin to connect to RE# pin to configure the echo function. If setting the CBUS pin to TXDEN by EEPROM programming, it will not support the RS485 echo function. If setting the CBUS pin to PWREN# by EEPROM programming, it will support the RS485 echo function.



A completed reference design example is given in Figure3-6

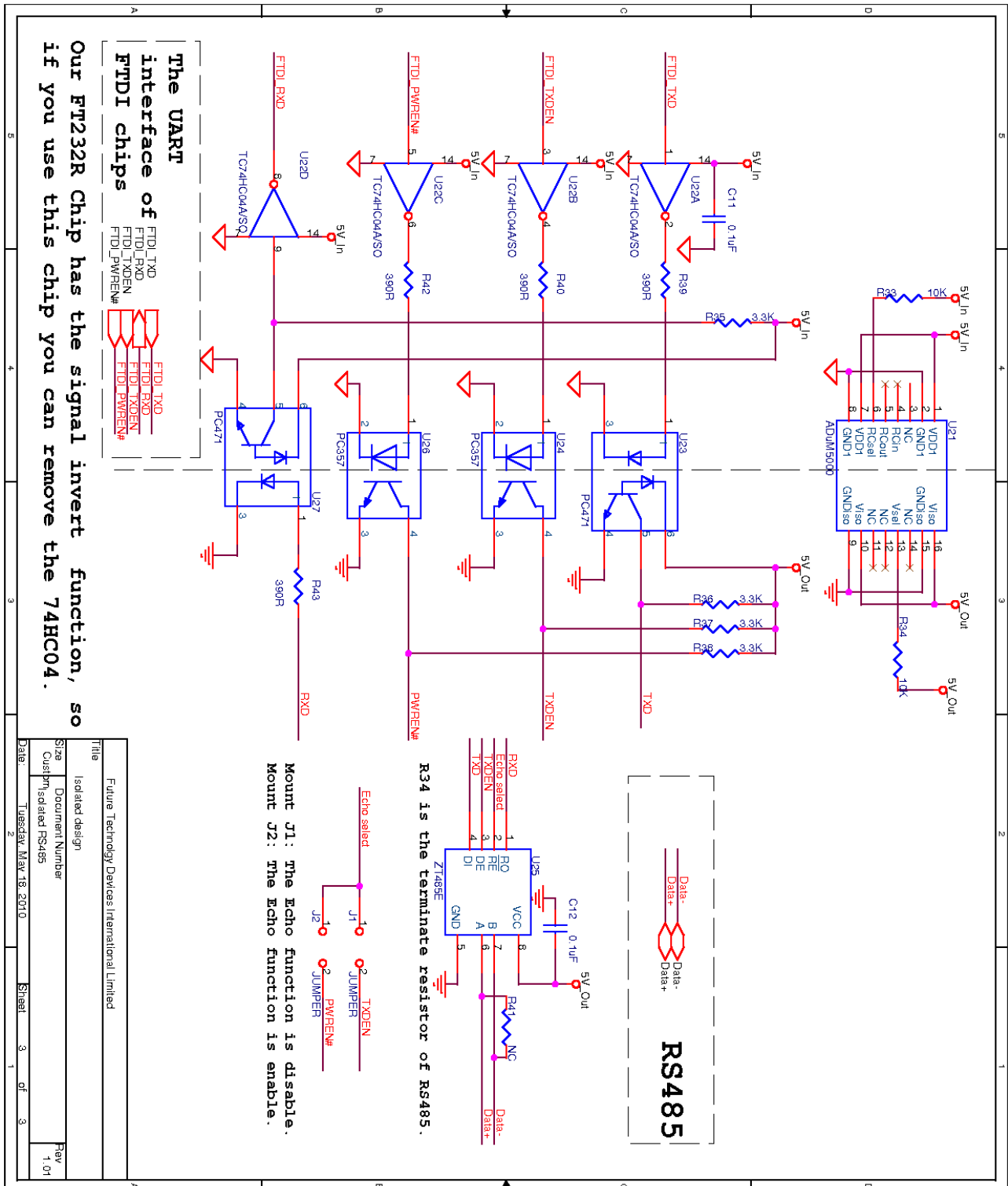

**Figure 3-6 Reference Design 5 – RS485 Isolation Implementation Example**

**Notes.**

1. The optical coupler inverts the signal and the data transfer also has a delay time. If this isolated example is used, then it is necessary to check the delay time and ensure that it has no side effects on the selected data baud rate.
2. FT232R support the ability to invert signals using the EEPROM setting. This allows removing the NOT gates used in the isolated examples.
3. When using FT232R and FT4232H in RS485 mode, it is necessary to program the EEPROM to enable the TXDEN function.

---

## 4 Contact Information

### Head Office – Glasgow, UK

Future Technology Devices International Limited  
Unit 1,2 Seaward Place, Centurion Business Park  
Glasgow G41 1HH  
United Kingdom  
Tel: +44 (0) 141 429 2777  
Fax: +44 (0) 141 429 2758

E-mail (Sales) [sales1@ftdichip.com](mailto:sales1@ftdichip.com)  
E-mail (Support) [support1@ftdichip.com](mailto:support1@ftdichip.com)  
E-mail (General Enquiries) [admin1@ftdichip.com](mailto:admin1@ftdichip.com)  
Web Site URL <http://www.ftdichip.com>  
Web Shop URL <http://www.ftdichip.com>

### Branch Office – Taipei, Taiwan

Future Technology Devices International Limited (Taiwan)  
2F, No. 516, Sec. 1, NeiHu Road  
Taipei 114  
Taiwan , R.O.C.  
Tel: +886 (0) 2 8791 3570  
Fax: +886 (0) 2 8791 3576

E-mail (Sales) [tw.sales1@ftdichip.com](mailto:tw.sales1@ftdichip.com)  
E-mail (Support) [tw.support1@ftdichip.com](mailto:tw.support1@ftdichip.com)  
E-mail (General Enquiries) [tw.admin1@ftdichip.com](mailto:tw.admin1@ftdichip.com)  
Web Site URL <http://www.ftdichip.com>

### Branch Office – Hillsboro, Oregon, USA

Future Technology Devices International Limited (USA)  
7235 NW Evergreen Parkway, Suite 600  
Hillsboro, OR 97123-5803  
USA  
Tel: +1 (503) 547 0988  
Fax: +1 (503) 547 0987

E-Mail (Sales) [us.sales@ftdichip.com](mailto:us.sales@ftdichip.com)  
E-Mail (Support) [us.support@ftdichip.com](mailto:us.support@ftdichip.com)  
Web Site URL <http://www.ftdichip.com>

### Branch Office – Shanghai, China

Future Technology Devices International Limited (China)  
Room 408, 317 Xianxia Road,  
Shanghai, 200051  
China  
Tel: +86 21 62351596  
Fax: +86 21 62351595

E-mail (Sales) [cn.sales@ftdichip.com](mailto:cn.sales@ftdichip.com)  
E-mail (Support) [cn.support@ftdichip.com](mailto:cn.support@ftdichip.com)  
E-mail (General Enquiries) [cn.admin@ftdichip.com](mailto:cn.admin@ftdichip.com)  
Web Site URL <http://www.ftdichip.com>

## **Distributor and Sales Representatives**

Please visit the Sales Network page of the FTDI Web site for the contact details of our distributor(s) and sales representative(s) in your country.

Vinculum is part of Future Technology Devices International Ltd. Neither the whole nor any part of the information contained in, or the product described in this manual, may be adapted or reproduced in any material or electronic form without the prior written consent of the copyright holder. This product and its documentation are supplied on an as-is basis and no warranty as to their suitability for any particular purpose is either made or implied. Future Technology Devices International Ltd will not accept any claim for damages howsoever arising as a result of use or failure of this product. Your statutory rights are not affected. This product or any variant of it is not intended for use in any medical appliance, device or system in which the failure of the product might reasonably be expected to result in personal injury. This document provides preliminary information that may be subject to change without notice. No freedom to use patents or other intellectual property rights is implied by the publication of this document. Future Technology Devices International Ltd, Unit 1, 2 Seaward Place, Centurion Business Park, Glasgow G41 1HH United Kingdom. Scotland Registered Number: SC136640

## **Appendix A – List of Figures and Tables**

### **List of Figures**

<b>Figure 2-1 RS232/RS422/RS485 Auto Sensing Block Diagram .....</b>	<b>4</b>
<b>Figure 2-2 Reference Design 1 – RS232/RS422/RS485 Auto-sensing .....</b>	<b>6</b>
<b>Figure 2-3 RS485/RS422 Auto-Sensing Block Diagram .....</b>	<b>7</b>
<b>Figure 2-4 Reference Design 2 – RS422/RS485 Auto-sensing .....</b>	<b>9</b>
<b>Figure 2-5 RS485's Termination Enable/Disable Control Circuit .....</b>	<b>10</b>
<b>Figure 3-1 Block Diagram of RS232 Isolated .....</b>	<b>11</b>
<b>Figure 3-2 Reference Design 3 – RS232 Isolation Implementation Example.....</b>	<b>12</b>
<b>Figure 3-3 Block Diagram of RS422 Isolated .....</b>	<b>13</b>
<b>Figure 3-4 Reference Design 4 – RS422 Isolation Implementation Example.....</b>	<b>14</b>
<b>Figure 3-5 Block Diagram of RS485 Isolated .....</b>	<b>15</b>
<b>Figure 3-6 Reference Design 5 – RS485 Isolation Implementation Example.....</b>	<b>16</b>

## Appendix B – Revision History

### Revision History

Version draft	Initial draft	04/05/2010
Version 1.0	First release	26/05/2010